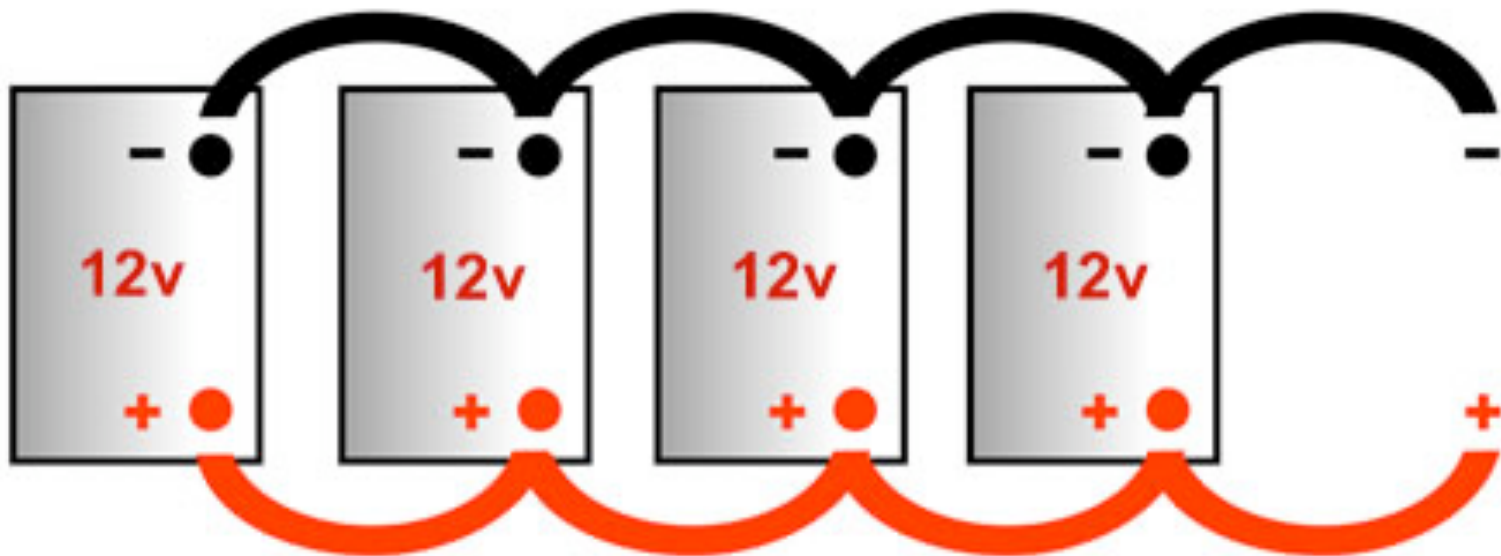


## Parallel Connection

QuickHowTo.Com



When all the positive terminals are connected in a line and all the negative terminals are connected in a line, this is called a parallel connection. In this case the voltage equal that of the highest battery. (12V)